

数字系统设计 第六次实验课

主要内容： lab6

Lab 6: Dedicate Microprocessor Lab

(2+2 hours)

Goal


To learn how to implement a dedicated microprocessor.

Procedure

- 1) Warm up: Implement the IF-THEN-ELSE example in Lecture 6 in your Basys 3 board. Connect the buttons and switches to the input pins of your module, and connect the leds to your output pins.
- 2) Manually design and implement on a FPGA a dedicated microprocessor to input one 8-bit value, and then determine whether the input value has an equal number of 0 and 1 bits. The microprocessor outputs a 1 if the input value has the same number of 0's and 1's; otherwise, it outputs a 0. For example, the number 10111011 will produce a 0 output; whereas, the number 001110011 will produce a 1 output. The algorithm is shown next. Draw the datapath and the corresponding FSM state diagram, FSM circuit, list the control words.

```
1   Count = 0           // for counting the number of 1 bits
2   INPUT N
3   WHILE (N ≠ 0) {
4       IF (N(0) = 1) THEN // least significant bit of N
5           Count = Count + 1
6       END IF
7       N = N >> 1       // shift N right one bit
8   }
9   OUTPUT (Count = 4) // output 1 if the test (Count = 4) is
                       true
```

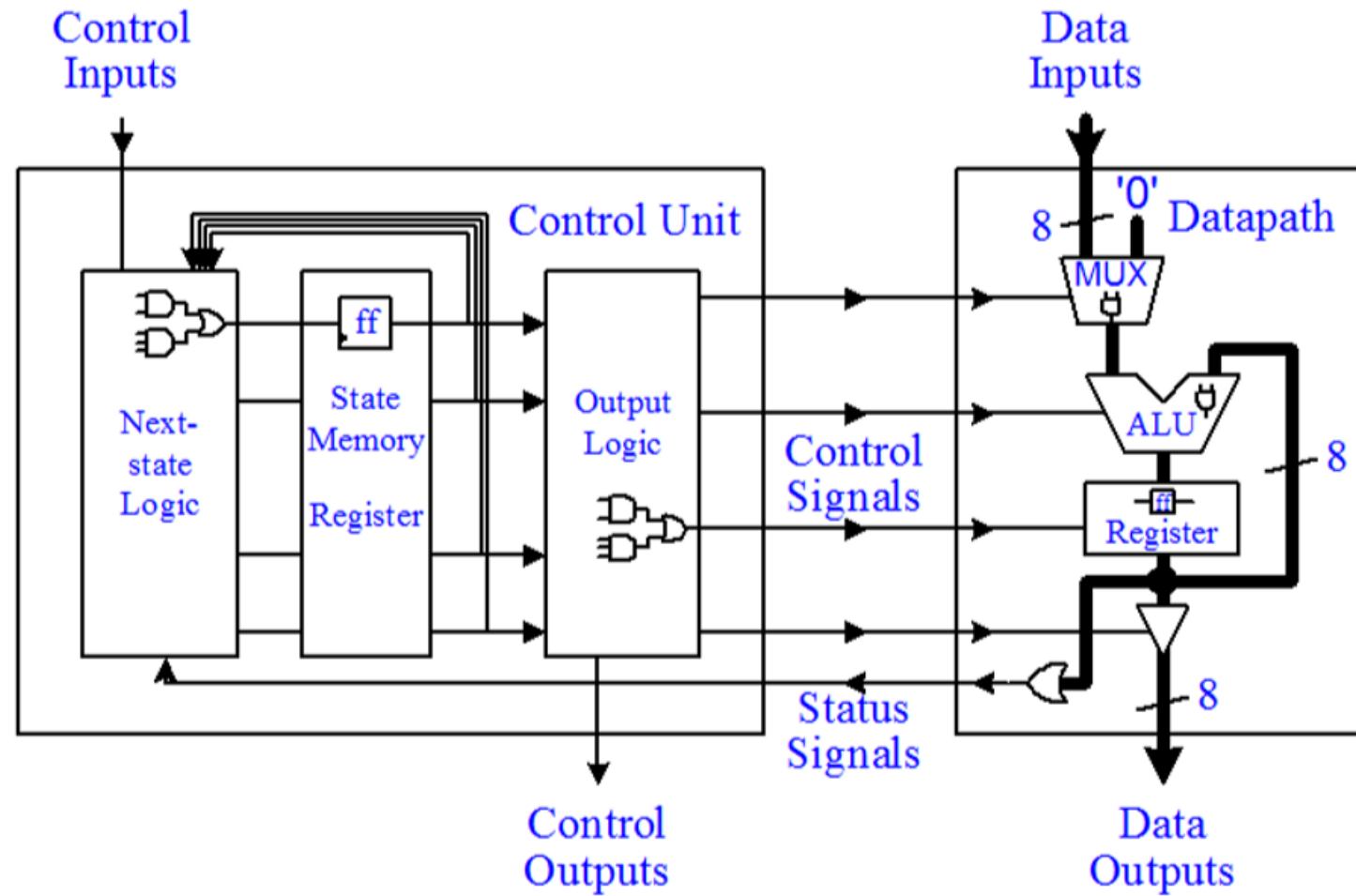- 3) Implement the datapath circuit and FSM circuit separately in Verilog module, connect them together by using a top module, and implement it in your Basys3 board. Connect the switches in board to your input pin, and connect the output pin to a LED.



Control unit

FSM输出控制字

Datapath

代码结构 (FSM+D)

- Control_Unit (FSM)
- DataPath (D)
- (TOP) MicroProcessor

- 2) Manually design and implement on a FPGA a dedicated microprocessor to input one 8-bit value, and then determine whether the input value has an equal number of 0 and 1 bits. The microprocessor outputs a 1 if the input value has the same number of 0's and 1's; otherwise, it outputs a 0. For example, the number 10111011 will produce a 0 output; whereas, the number 00110011 will produce a 1 output. The algorithm is shown next. Draw the ~~datapath~~ and the corresponding FSM state diagram, FSM circuit, list the control words.

```
1      Count = 0                // for counting the number of 1 bits
2      INPUT N
3      WHILE (N ≠ 0) {
4          IF (N(0) = 1) THEN // least significant bit of N
5              Count = Count + 1
6          END IF
7          N = N >> 1           // shift N right one bit
8      }
9      OUTPUT (Count = 4) // output 1 if the test (Count = 4) is
                           true
```


step1: 画出数据通路

step2: 控制单元: 画出状态转换图

step3: 控制单元: 输出控制字

step1: 画出数据通路


确定器件

 

```
Count = 0 //  
INPUT N  
WHILE ( $N \neq 0$ ) {  
    IF ( $N(0) = 1$ ) THEN /.  
        Count = Count + 1 +  
    END IF  
     $N = N >> 1$  /.  
}  
OUTPUT (Count = 4) // ou
```

- 两个Register (count、N)
- 一个移位寄存器
- 一个加法器
- ? 个mux
- 其他

连线

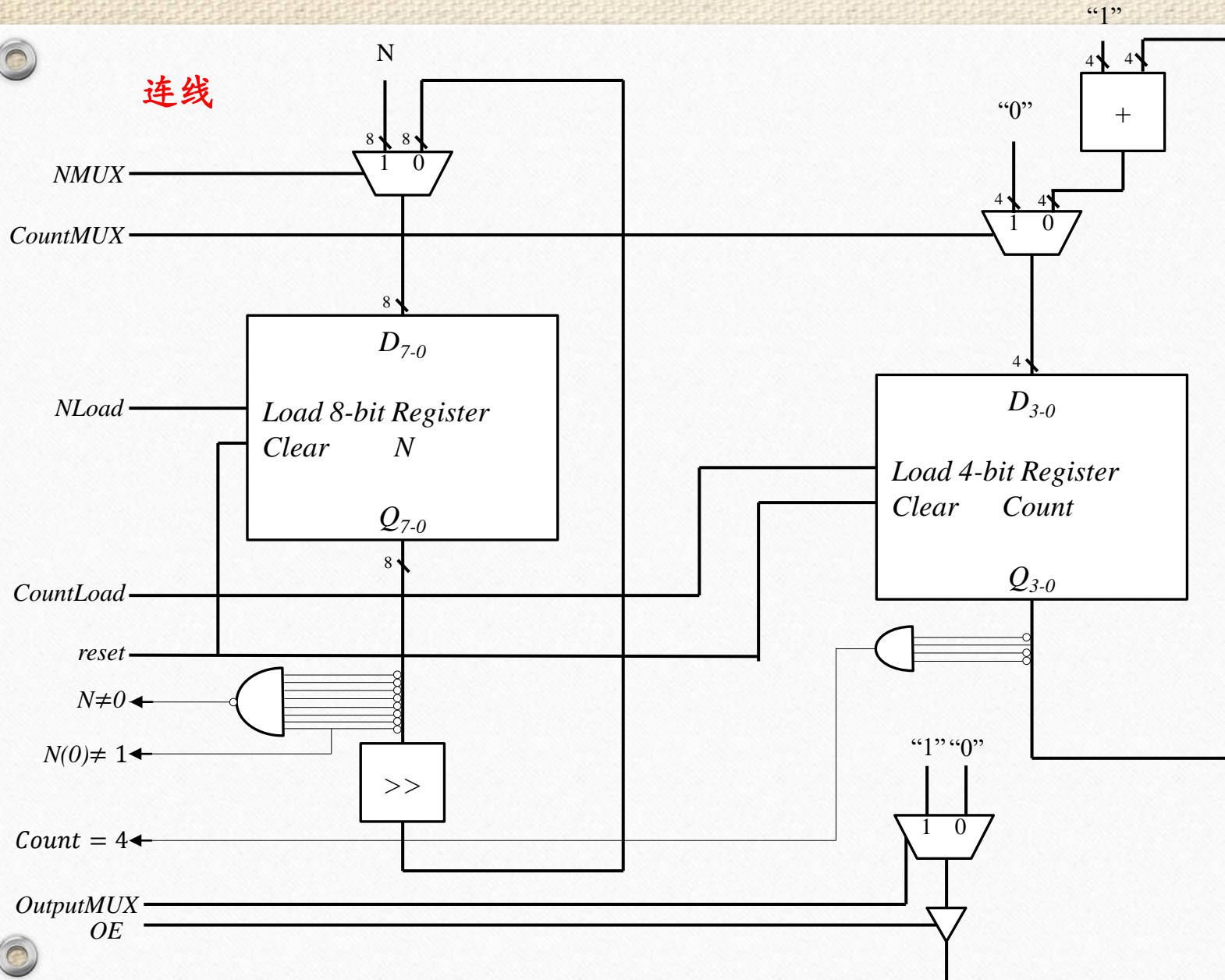


```

Count = 0 //
INPUT N
WHILE (N ≠ 0) {
    IF (N(0) = 1) THEN /
        Count = Count + 1
    END IF
    N = N >> 1 /
}
OUTPUT (Count = 4) // ou


```


step2: 画出状态转换图 (控制单元)

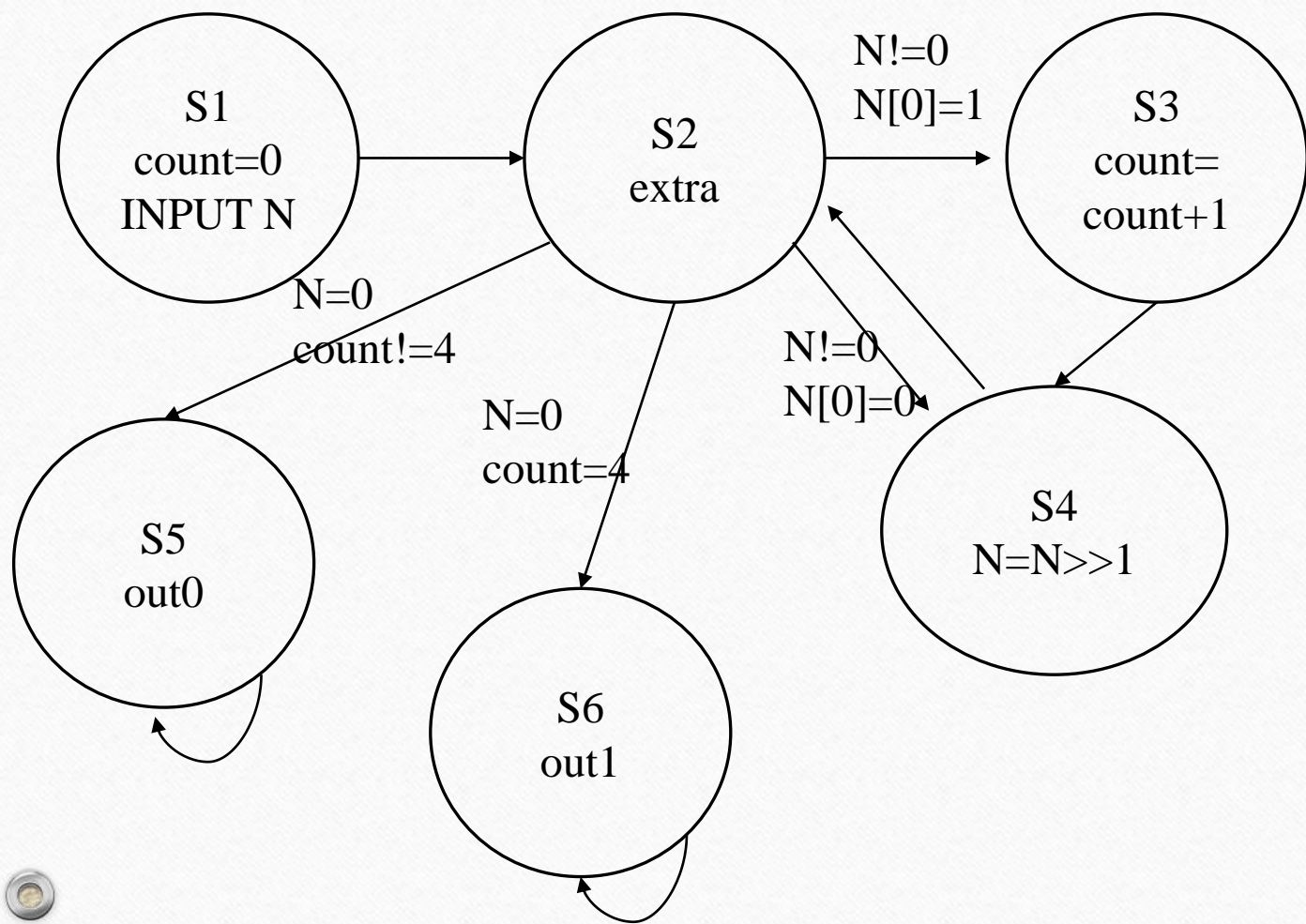



```
Count = 0 //  
INPUT N //  
WHILE (N ≠ 0) { //  
    IF (N(0) = 1) THEN //  
        Count = Count + 1 //  
    END IF //  
    N = N >> 1 //  
} //  
OUTPUT (Count = 4) // ou
```

step2: 画出状态转换图 (控制单元)

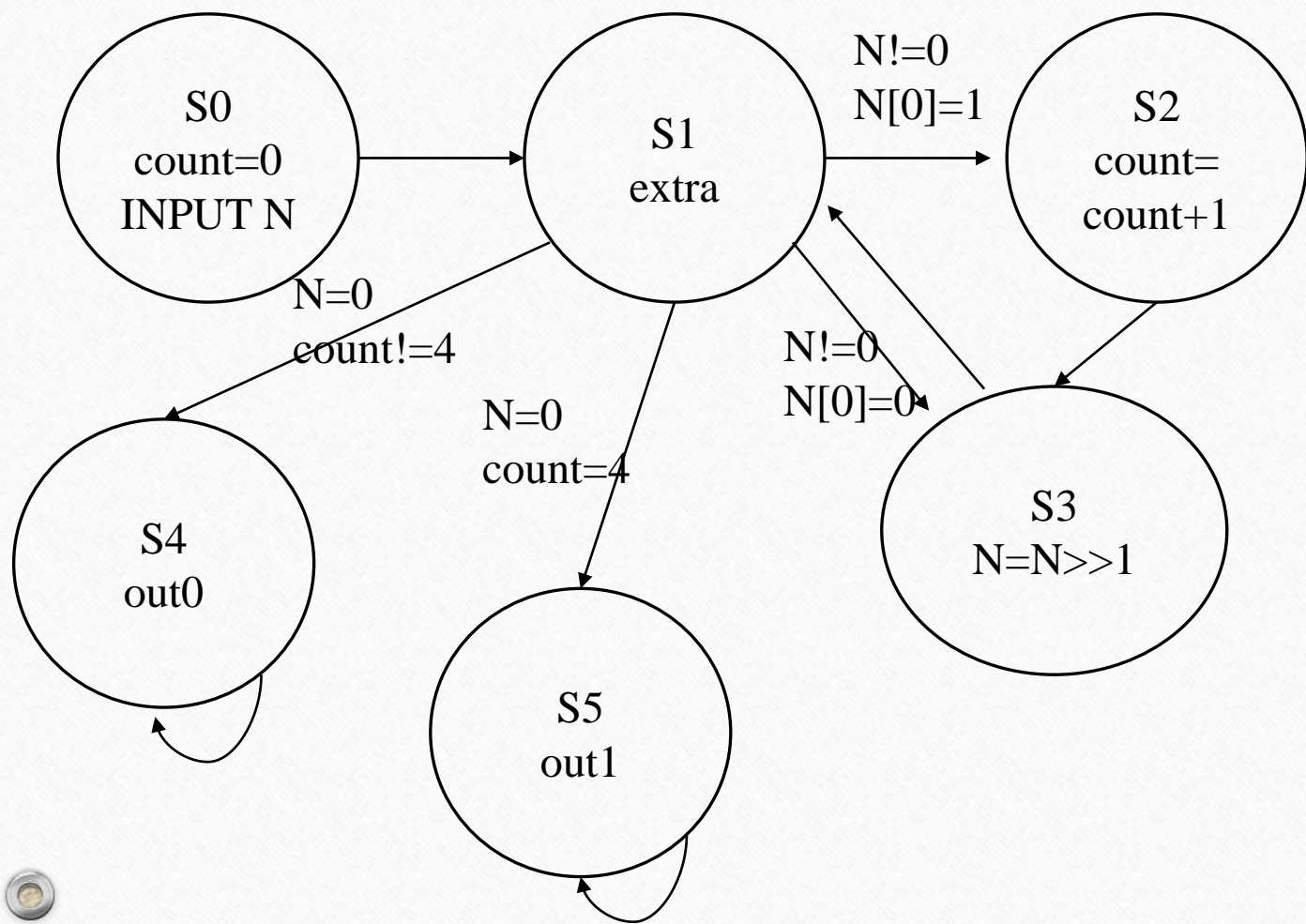

```
Count = 0 //  
INPUT N //  
WHILE (N ≠ 0) { //  
    IF (N(0) = 1) THEN //  
        Count = Count + 1 //  
    END IF //  
    N = N >> 1 //  
} //  
OUTPUT (Count = 4) // ou
```


step3: 输出控制字 (控制单元)

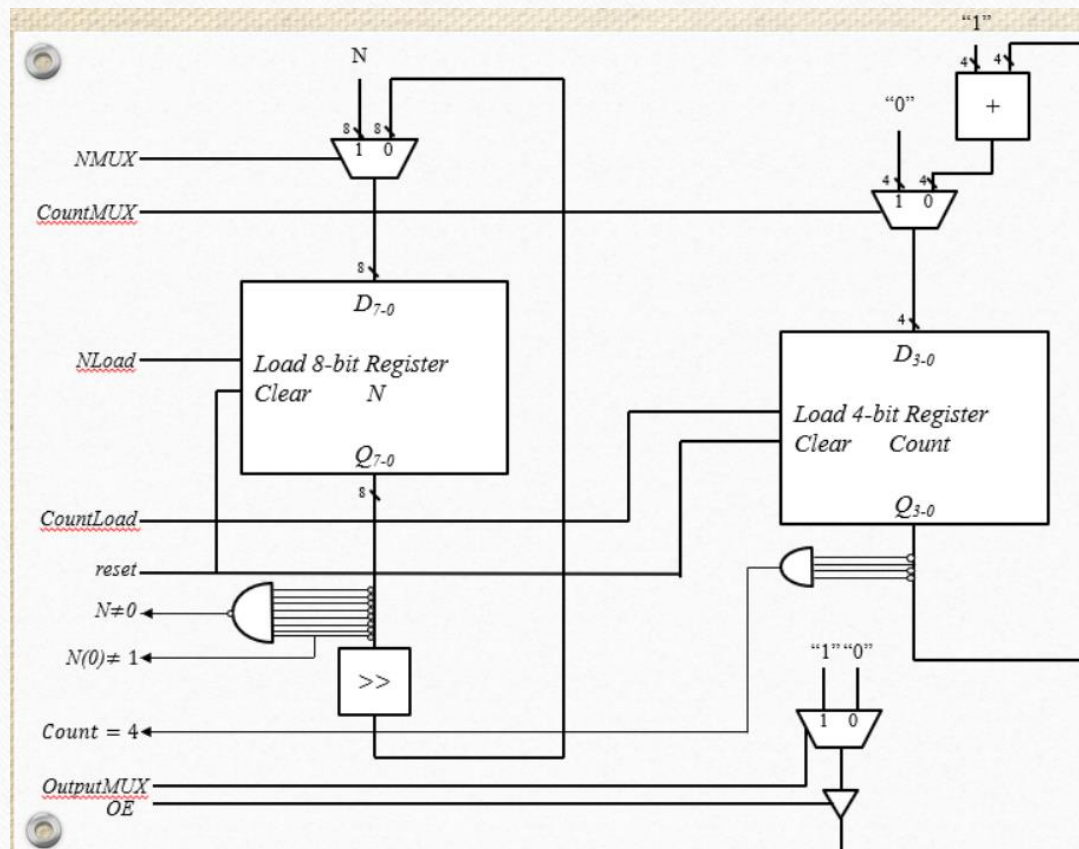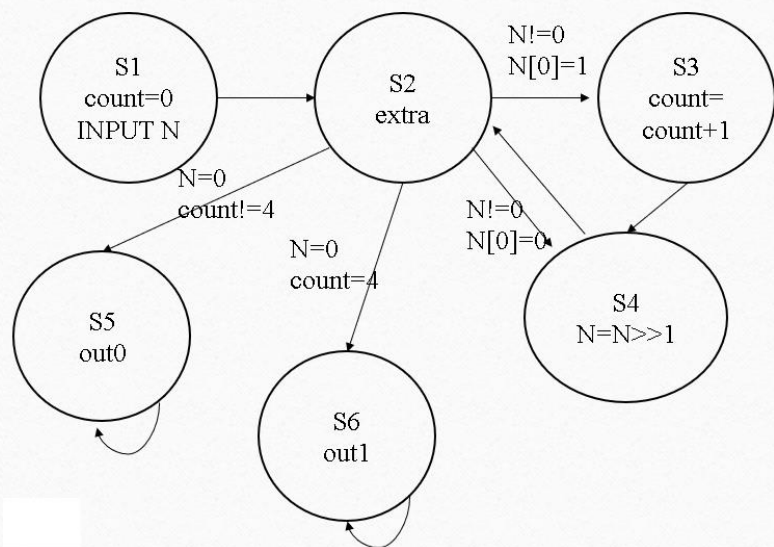

状态反馈信号(count, N) 状态转换 数据通路 控制字

step3: 输出控制字 (控制单元)

- 根据数据通路所需、确定每个状态的控制字

step3: 输出控制字 (控制单元)

	<i>NMUX</i>	<i>CountMUX</i>	<i>NLoad</i>	<i>CountLoad</i>	<i>OutputMUX</i>	<i>OE</i>
<i>S1</i> count=0 INPUT N	<i>1</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>X</i>	<i>0</i>
<i>S2</i> extra	<i>X</i>	<i>X</i>	<i>0</i>	<i>0</i>	<i>X</i>	<i>0</i>
<i>S3</i> count= count+1	<i>X</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>X</i>	<i>0</i>
<i>S4</i> N=N>>1	<i>0</i>	<i>X</i>	<i>1</i>	<i>0</i>	<i>X</i>	<i>0</i>
<i>S5</i> out0	<i>X</i>	<i>X</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>1</i>
<i>S6</i> out1	<i>X</i>	<i>X</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>1</i>

要点：

- 根据数据通路，搭建datapath模块(组合逻辑)
- 根据状态转换图写有限状态机（control unit模块），每个状态下输出特定控制字（时序逻辑）
- 用一个顶层模块将control unit模块和datapath模块连接起来。

要求：

- 实验报告（状态图、datapath、control word、仿真和实验结果）
- 验收

顶层代码

```
module Dedicate_Microprocessor(  
    input clk,  
    input reset,  
    input [7:0] N,  
    // output [7:0] check,  
    output led  
);  
  
    wire NMUX, CountMUX, NLoad, CountLoad, OE, OutputMUX;  
    wire NnotOne, NnotZero, CountFour;  
  
    Control c1(.clk(clk), .rst(reset), .NnotZero(NnotZero), .NnotOne(NnotOne), .C  
  
    Datapath d1(.clk(clk), .N(N), .rst(reset), .NMUX(NMUX), .CountMUX(CountMUX),  
  
    // assign check = N;  
  
endmodule
```


寄存器代码

```
always @(posedge clk or posedge rst) begin  
  
    if(rst) out <= 0;  
    else if(load) out <= ina;  
  
end
```

移位代码

```
assign shiftedN = preN >> 1;
```